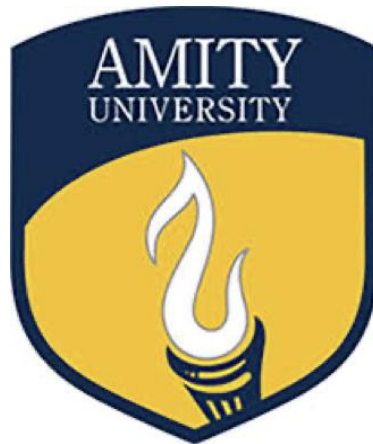


Lab File
On
Digital Electronics And Computer Organisation

Submitted To
Ms Neha Arora
Amity University Uttar Pradesh



In partial fulfilment of the requirements for the award degree of
Bachelor of Technology
In
Artificial Intelligence
by
DEVANSHU KUMAR SINGH
A023119820024

DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING
AMITY SCHOOL OF ENGINEERING AND TECHNOLOGY
AMITY UNIVERSITY UTTAR PRADESH
NOIDA (U.P)

INDEX

S NO	AIM	DATE	FACULTY'S SIGNATURE
1	Verification and interpretation of truth tables for various logical gates.	07-01-2022	
2			
3			
4			
5			
6			
7			
8			
9			
10			

Experiment Number: 1

AIM: Verification and interpretation of truth tables for various logical gates.

PLATFORM/TOOLS USED:

1. Virtual Lab
2. circuitverse.org

THEORY:

Logic gates are the basic building blocks of any digital system. Logic gates are electronic circuits having one or more than one input and only one output. The relationship between the input and the output is based on a certain logic. Based on this, logic gates are named as

- | | |
|--------------|----------------|
| a. AND gate | e. NOR gate |
| b. OR gate | f. Ex-OR gate |
| c. NOT gate | g. Ex-NOR gate |
| d. NAND gate | |

1. AND gate:

Truth table

A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1

KMAP

A\B	0	1
0	0	0
1	0	1

Expression: $Y=A.B$

Symbol:



IC No: 7408

2. OR gate:

Truth table

A	B	$Y=A+B$
0	0	0
0	1	1

1	0	1
1	1	1

KMap

A\B	0	1
0	0	1
1	1	1

Expression: $Y=A+B$

Symbol:



IC No: 7432

3. NOT gate:

Truth table

A	Y
0	1
1	0

Expression: $Y=A+B$

Symbol:



IC No: 7404

4. NAND gate:

Truth table

A	B	$Y=(AB)'$
0	0	1
0	1	1
1	0	1
1	1	0

KMap

A\B	0	1
0	1	1
1	1	0

Expression: $Y=(AB)'$

Symbol:



IC No: 7400

5. NOR gate:

Truth table


A	B	$Y=(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

KMap

A\B	0	1
0	1	0
1	0	0

Expression: $Y=(A+B)'$

Symbol:

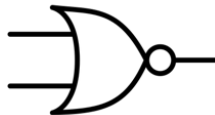

IC No: 7402

6. XOR gate

Truth table

A	B	$Y=A.B$
0	0	0


0	1	1
1	0	1
1	1	0

KMap

A\B	0	1
0	0	1
1	1	0

Expression: $Y = A \oplus B$

Symbol:

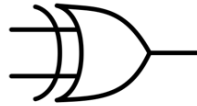

IC No: 7486

7. XNOR gate

Truth table


A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

KMap


A\B	0	1
0	1	0
1	0	1

Expression: $Y = A \odot B$

Symbol:

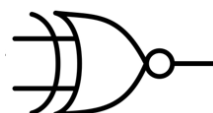

RESULT:

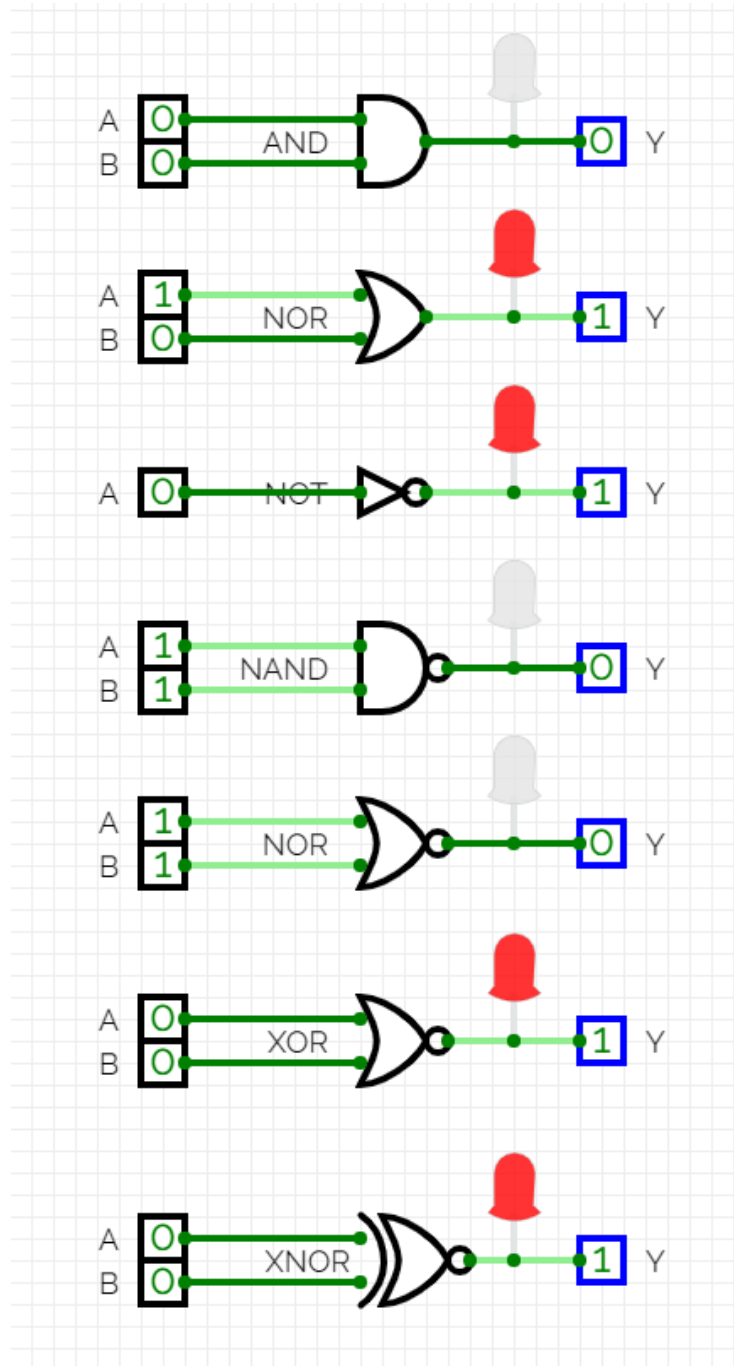

CONCLUSIONS: The logic and universal gates' truth tables are verified.

CRITERIA	TOTAL MARKS	MARKS OBTAINED	COMMENTS
Concept (A)	2		
Implementation (B)	2		
Performance (C)	2		
TOTAL	6		